

## NCR CAMPUS, MODINAGAR

### DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

Analog and Digital Electronics Laboratory (18CSS201J)

Title of Experiment	: <b><u>Experiment No. 3 : Square/Rectangular Waveform Generator</u></b>
Name of the candidate	: ANANYA GUYPTA
Register Number	: RA1911003030265
Branch-Section	: CSE-I

#### **Experiment No. 3 : Square/Rectangular Waveform Generator**

**Aim:** Design and implement using simulator a Square/rectangular waveform generator (Op-Amp relaxation oscillator).

**Apparatus Require:**

LM 741/OP27 or its equivalent  
Capacitor – 0.1 $\mu$ F  
Resistors – 10K $\Omega$  (2), 1K $\Omega$  (2)  
AD Kit  
Bread Board.

**Theory:**

The non-sinusoidal waveform generators are also called relaxation oscillators. The op-amp relaxation oscillator shown in figure is a square wave generator. In general, square waves are relatively easy to produce.

The comparator uses positive feedback that increases the gain of the amplifier. In a comparator circuit this offers two advantages. First, the high gain causes the op-amp's output to switch very quickly from one state to another and vice-versa. Second, the use of positive feedback gives the circuit hysteresis. In the op-amp square-wave generator circuit given in figure, the output voltage  $v_{out}$  is shunted to ground by two Zener diodes  $Z_1$  and  $Z_2$  connected back-to-back and is limited to either  $V_{Z2}$  or  $-V_{Z1}$ . A fraction of the output is fed back to the non-inverting (+) input terminal. Combination of  $R_f$  and  $C$  acting as a low-pass R-C circuit is used to integrate the output voltage  $v_{out}$  and the capacitor voltage  $v_c$  is applied to the inverting input terminal in place of external signal.

The differential input voltage is given as  $v_{in} = v_c - \beta v_{out}$

When  $v_{in}$  is positive,  $v_{out} = -V_{Z1}$  and when  $v_{in}$  is negative  $v_{out} = +V_{Z2}$ . Consider an instant of time when  $v_{in} < 0$ . At this instant  $v_{out} = +V_{Z2}$ , and the voltage at the non-inverting (+) input terminal is  $\beta V_{Z2}$ , the capacitor  $C$  charges exponentially towards  $V_{Z2}$ , with a time constant  $R_f C$ .

The output voltage remains constant at  $V_{Z2}$  until  $v_c$  equals  $\beta V_{Z2}$ .

When it happens, comparator output reverses to  $-V_{Z1}$ . Now  $v_c$  changes exponentially towards  $-V_{Z1}$  with the same time constant and again the output makes a transition from  $-V_{Z1}$  to  $+V_{Z2}$  when  $v_c$  equals  $-\beta V_{Z1}$ .

Let  $V_{Z1} = V_{Z2}$

The time period,  $T$ , of the output square wave is determined using the charging and discharging phenomena of the capacitor  $C$ . The voltage across the capacitor,  $v_c$  when it is charging from  $-\beta V_Z$  to  $+V_Z$  is given by

$$V_c = [1 - (1 + \beta)]e^{-T/2\tau}$$

Where  $\tau = R_f C$

The waveforms of the capacitor voltage  $v_c$  and output voltage  $v_{out}$  (or  $v_z$ ) are shown in figure.


When  $t = T/2$

$$V_c = +\beta V_Z \text{ or } +\beta V_{out}$$

$$\text{Therefore } \beta V_Z = V_Z [1 - (1 + \beta)e^{-T/2\tau}]$$

$$\text{Or } e^{-T/2\tau} = 1 - \beta/1 + \beta$$

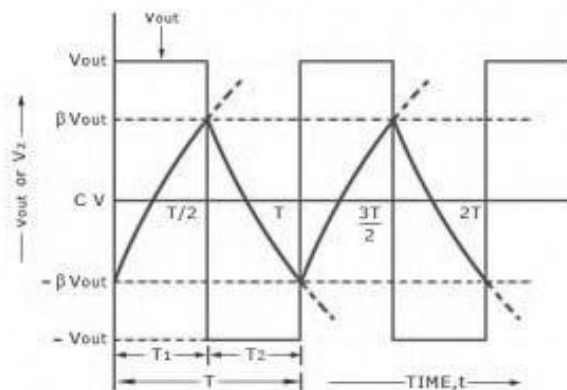
$$\text{Or } T = 2\tau \log_e 1 + \beta/1 - \beta = 2R_f C \log_e [1 + (2R_3/R_2)]$$



The frequency,  $f = 1/T$ , of the square-wave is independent of output voltage  $V_{out}$ . This circuit is also known as free-running or astable multivibrator because it has two

**quasi-stable states.** The output remains in one state for time  $T_1$  and then makes an abrupt transition to the second state and remains in that state for time  $T_2$ . The cycle repeats itself after time  $T = (T_1 + T_2)$  where  $T$  is the time period of the square-wave. The op-amp square-wave generator is useful in the frequency range of about 10 Hz -10 kHz. At higher frequencies, the op-amp's slew rate limits the slope of the output square wave. The symmetry of the output waveform depends on the matching of two Zener diodes  $Z_1$  and  $Z_2$ . The unsymmetrical square-wave ( $T_1$  not equal to  $t_2$ ) can be had by using different constants for charging the capacitor  $C$  to  $+V_{out}$  and  $-V_{out}$

### Circuit Diagram:

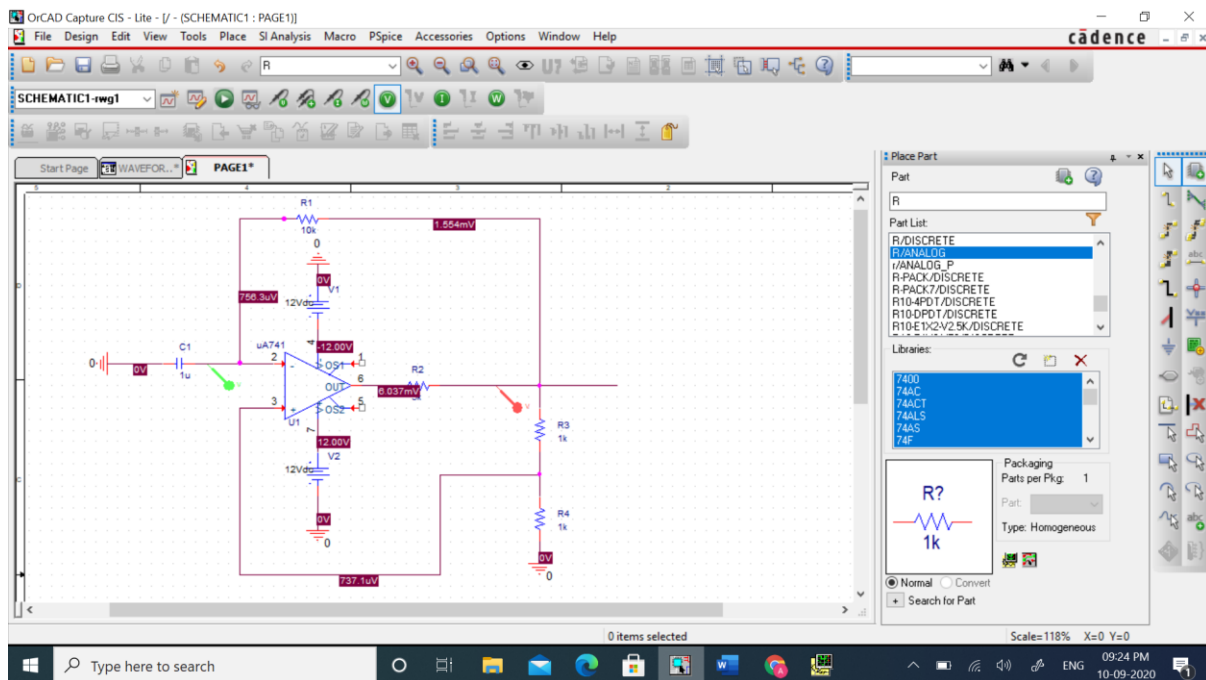

### Procedure:

1. Expression for the frequency of oscillation,  

$$f = 1 / (2RC \log_e (1 + \beta / (1 - \beta)))$$
, where  $\beta = (R_3 / (R_3 + R_2))$ .
2. Choose any frequency between 1 kHz and 5 kHz and select the values of  $R_1$ ,  $R_2$ ,  $R$ , and  $C$ .
3. Connect the circuit as per the circuit diagram and give the supply volt age.
4. Observe the frequency of operation of the circuit and compare with the theoretical values.
5. Change the  $R$  and  $C$  values to change the frequency and oscillation and verify with the theoretical values.
6. Trace the output waveform for inverting and non-inverting inputs.

### Graphs:

